

1h.) 1.)  $Z_{er}$  berechnen:

$$\frac{\left(sL + \frac{1}{sC_2}\right) \cdot \frac{1}{sC_1}}{sL + \frac{1}{sC_2} + \frac{1}{sC_1}} = \frac{\frac{sLC_2 + 1}{s^2C_1C_2}}{\frac{s^3C_1C_2L + sC_1 + sC_2}{s^2C_1C_2}} = \frac{s^2LC_2 + 1}{s^3C_1C_2L + sC_1 + sC_2} = Z_{er}$$

2.) Spannungsteiler für gesamte Schaltung

$$\frac{U_c}{U_e} = \frac{Z_{er}}{R + Z_{er}} \Rightarrow \frac{Z_{er}}{R + Z_{er}} \cdot U_e = U_c$$

3.) Spannungsteiler für  $Z_{er}$

$$\frac{U_a}{U_c} = \frac{U_a}{U_e \cdot \frac{Z_{er}}{Z_{er} + R}} = \frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + sL} \Rightarrow$$

$$\frac{U_a}{U_e} = \frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + sL} \cdot \frac{Z_{er}}{R + Z_{er}} = \frac{(s^2C_2L + 1) \cdot Z_{er}}{R + Z_{er}}$$

$$\Rightarrow \frac{U_a}{U_e} = \frac{1}{(s^2C_2L + 1)} \cdot \frac{(s^2C_2L + 1)}{R + \frac{s^2C_2L + 1}{s^3C_1C_2L + sC_1 + sC_2}}$$



$$\Rightarrow \frac{U_a}{U_e} = \frac{1}{R \cdot (s^3C_1C_2L + sC_1 + sC_2) + s^2C_2L + 1} = \frac{1}{\underbrace{s^3C_1C_2RL}_1 + s \cdot \underbrace{(C_1R + C_2R)}_2 + \underbrace{s^2LC_2 + 1}_1}$$

$$H(s) = \frac{1}{s^3 + 2s + s^2 + 1}$$

140) Betrag:

$$H(s) = \frac{1}{s^3 + s^2 + 2s + 1} \quad s = j\omega$$

$$|H(j\omega)| = \frac{1}{\sqrt{(-\omega^2 + 1)^2 + (2j\omega - j\omega^3)^2}} = \frac{1}{\sqrt{-\omega^6 + 4\omega^4 - 6\omega^2 + 1}}$$

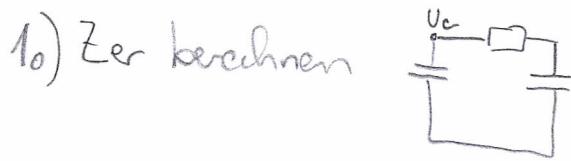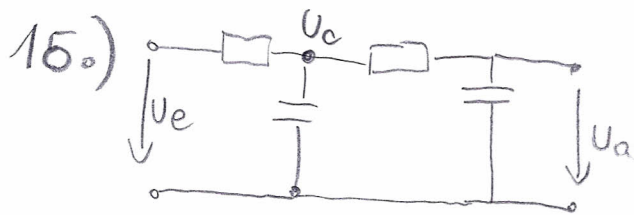

$$Z_{er} = \frac{\left(R + \frac{1}{sC}\right) \cdot \frac{1}{sC}}{\frac{1}{sC} + \frac{1}{sC} + R} = \frac{\frac{sCR + 1}{s^2 C^2}}{\frac{2 + sCR}{sC}} = \frac{sCR + 1}{sC \cdot (2 + sCR)}$$

2.) Spannungsteiler für gesamte Schaltung

$$\frac{U_c}{U_e} = \frac{Z_{er}}{Z_{er} + R} \Rightarrow U_c = U_e \cdot \frac{Z_{er}}{Z_{er} + R}$$

3.) Spannungsteiler für  $Z_{er}$

$$\frac{U_a}{U_c} \Rightarrow \frac{U_a}{U_e \cdot \frac{Z_{er}}{Z_{er} + R}} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \Rightarrow \frac{U_a}{U_e} = \frac{1 \cdot Z_{er}}{(sCR + 1) \cdot (Z_{er} + R)}$$

$$\frac{U_a}{U_e} = \frac{1}{sCR + 1} \cdot \frac{\frac{sCR + 1}{sC \cdot (2 + sCR)}}{\frac{(sCR + 1) + sCR \cdot (2 + sCR)}{sC \cdot (2 + sCR)}}$$

$$\frac{U_a}{U_e} = \frac{1}{sCR + 1 + 2sCR + s^2 C^2 R^2} = \frac{1}{s^2 C^2 R^2 + 3sCR + 1}$$

$$\Rightarrow \frac{U_a(s)}{U_e(s)} = \frac{1}{s^2 + 3s + 1}$$